

Detailed Analysis of the Digital Error Correction in the Pipelined ADC

Pengyu Zeng
zpyeis@whu.edu.cn

Introduction

- Digital error correction is one of the most crucial algorithms in the pipelined ADC. The structure of the ADC depends on this algorithm which can correct the aperture error and the digital output error caused by the mismatch of comparators.
- There are many different methods to analysis this algorithm presented in previous works. Meanwhile, there are many details need to be interpreted.
- This report tries to integrate different methods and proposes the detailed analysis on the basic thinking of the pipelined ADC, the principal of the digital error correction algorithm and the significant points in the valid algorithm.

Outline

- The physical model of the pipelined ADC
- The basic pipelined ADC
- Redundancy and digital error correction
- Comparator offset and digital output

Outline


- Key points

- The physical model of the pipelined ADC
- The basic pipelined ADC
- Redundancy and digital error correction
- Comparator offset and digital output


- To build:
 - Physical model
 - Circuits
 - Math expression
- Analysis the algorithm with the math expression

Physical Model

 
- Basic ADC (Flash)
- k bit Need $2^k - 1$ comparators



Physical Model

 


- 15 Comparators

 

- Step by step
 - Coarse quantize
 - Get the **residue**
 - Amplify and quantize
- $2 \times 3 = 6$ Comparators

Physical Model

- The Thinking of the Pipelined ADC

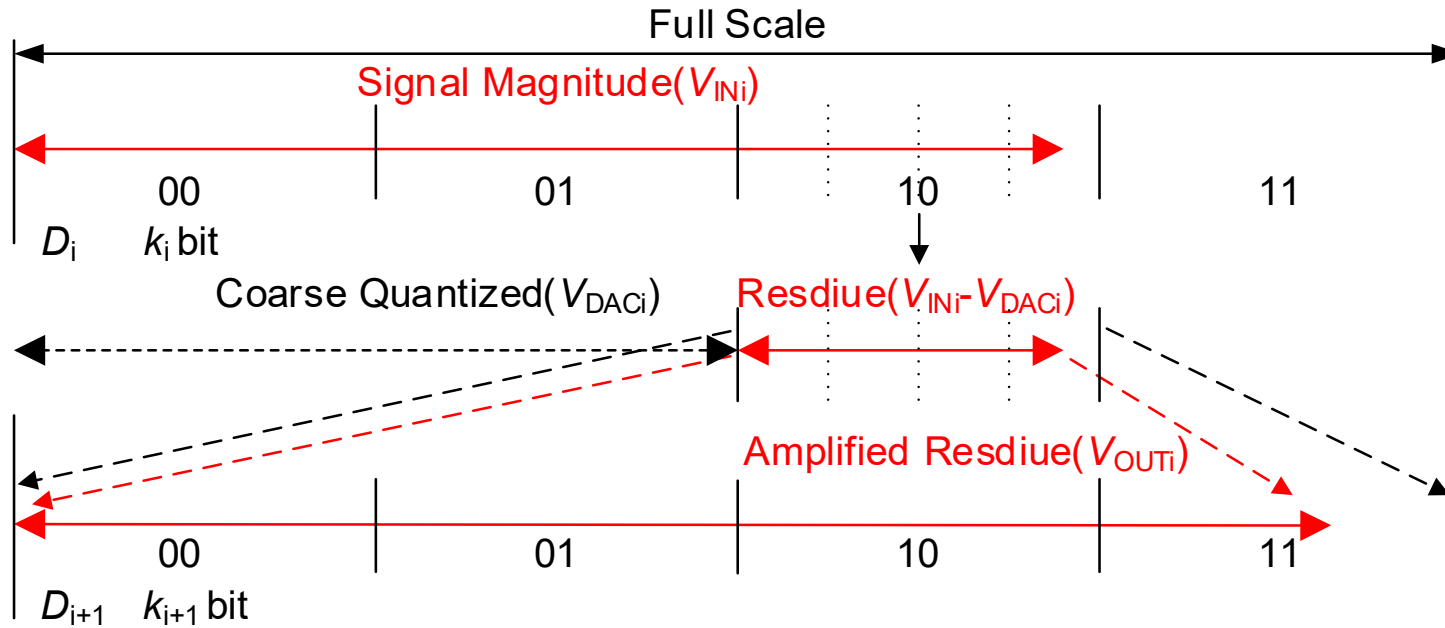


- Step by step
 - Coarse quantize
 - Get the **residue**
 - Amplify and quantize

$$V_{OUTi} = G_i(V_{RESi}) = G_i(V_{INi} - D_i LSB_i) \quad LSB_i = \frac{FS}{2^{k_i}}$$

$$V_{RESi} < LSB_i \quad G_i = 2^{k_i}$$

Physical Model

- The Transfer Waveform

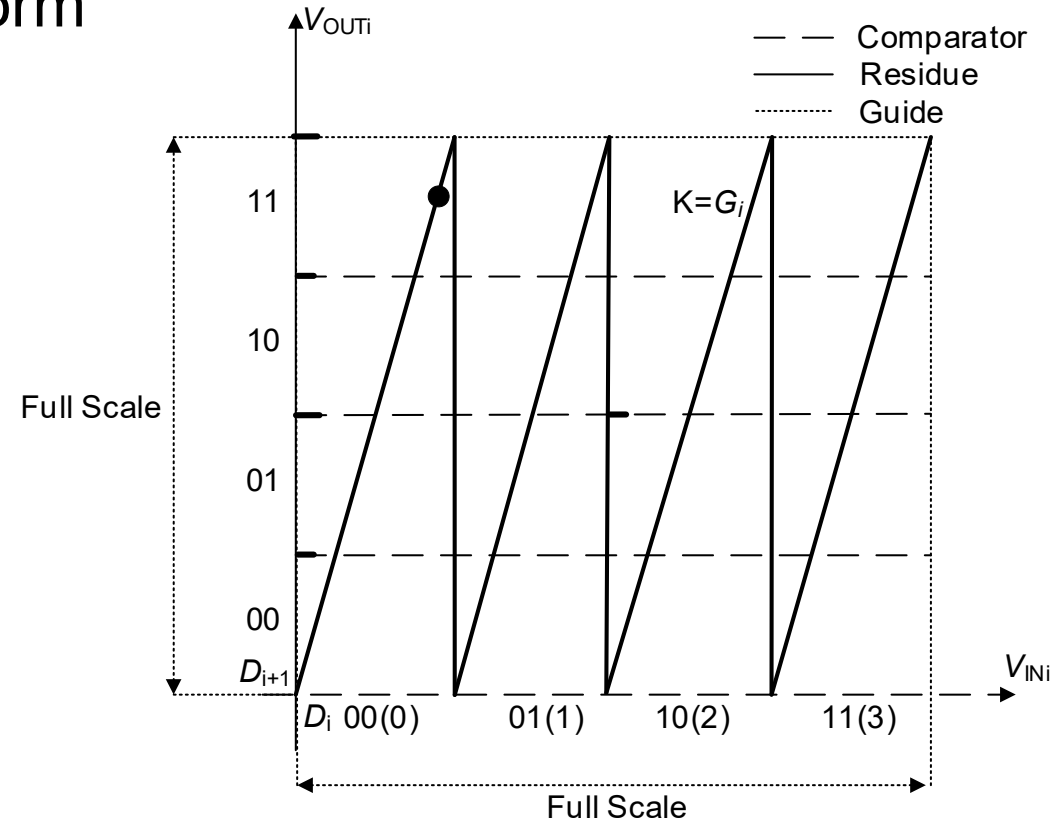


$$V_{OUTi} = G_i(V_{RESi}) = G_i(V_{INi} - D_i LSB_i) \quad LSB_i = \frac{FS}{2^{k_i}}$$

$$V_{RESi} < LSB_i \quad G_i = 2^{k_i}$$

Physical Model

- Digital Output of the Pipelined ADC

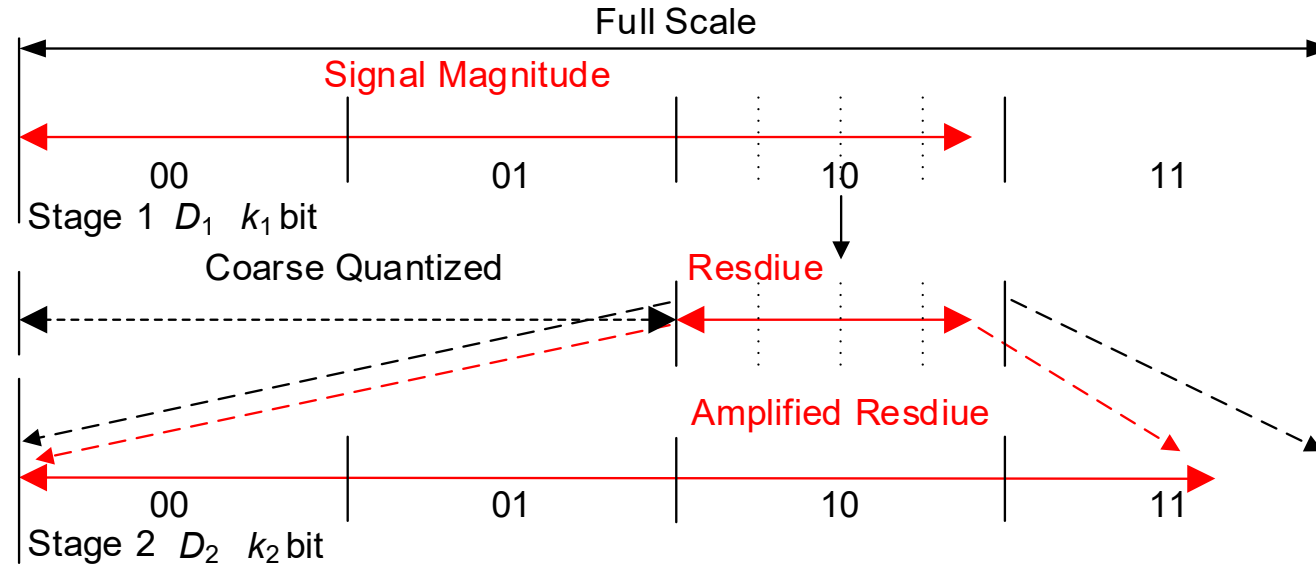


Stage 1: 10

Stage 2: 11

Why? System output : 1011

Physical Model

- Digital Output

 


- A_{OUT} is the analog output of the ADC, *error* is the system quantization error

$$V_{IN} = A_{OUT} + \text{error} \quad A_{OUT} = D_{OUT} LSB = \sum_{n=1}^{i-1} \frac{A_{OUTi}}{\prod_{n=1}^{i-1} G_n} = \sum_{n=1}^{i-1} \frac{D_i LSB_i}{\prod_{n=1}^{i-1} G_n} = \frac{D_1 LSB_1}{1} + \frac{D_2 LSB_2}{G_1}$$

Physical Model

- Digital Output

 


- A_{OUT} is the analog output of the ADC, *error* is the system quantization error

$$V_{IN} = A_{OUT} + \text{error} \quad A_{OUT} = D_{OUT} LSB = \sum_{i=1}^N \frac{A_{OUTi}}{\prod_{n=1}^{i-1} G_n} = \sum_{i=1}^N \frac{D_i LSB_i}{\prod_{n=1}^{i-1} G_n} = \frac{D_1 LSB_1}{1} + \frac{D_2 LSB_2}{G_1}$$

- Actually, A_{OUTi} is equal to V_{DACi}

Physical Model

- Digital Output

 


$$A_{\text{OUT}} = D_{\text{OUT}} \text{LSB} = \frac{D_1 \text{LSB}_1}{1} + \frac{D_2 \text{LSB}_2}{G_1} \quad \text{LSB}_i = \frac{FS}{2^{k_i}}$$

$$A_{\text{OUT}} = D_1 \frac{FS}{2^{k_1}} + D_2 \frac{FS}{G_1 2^{k_2}} = D_1 G_1 2^{k_2 - k_1} \text{LSB} + D_2 \text{LSB} = (D_1 G_1 2^{k_2 - k_1} + D_2) \text{LSB}$$

LSB

Physical Model

- Digital Output

 

$$A_{\text{OUT}} = D_{\text{OUT}} \text{LSB} = \frac{D_1 \text{LSB}_1}{1} + \frac{D_2 \text{LSB}_2}{G_1}$$


$$A_{\text{OUT}} = D_1 \frac{FS}{2^{k_1}} + D_2 \frac{FS}{G_1 2^{k_2}} = D_1 G_1 2^{k_2 - k_1} \text{LSB} + D_2 \text{LSB} = (D_1 G_1 2^{k_2 - k_1} + D_2) \text{LSB}$$

$$A_{\text{OUT}} = D_{\text{OUT}} \text{LSB} = (G_1 2^{k_2 - k_1} D_1 + D_2) \text{LSB}$$

$$D_{\text{OUT}} = G_1 2^{k_2 - k_1} D_1 + D_2$$

Physical Model

- Digital Output

 

$$D_{\text{OUT}} = G_1 2^{k_2 - k_1} D_1 + D_2$$

$$G_1 = 2^{k_1} \quad D_{\text{OUT}} = 2^{k_2} D_1 + D_2$$


$$D_{\text{OUT}} = D_1 \ll k_2 + D_2$$

Stage 1: 10

Stage 2: 11


Output : 1011

Basic Pipelined ADC

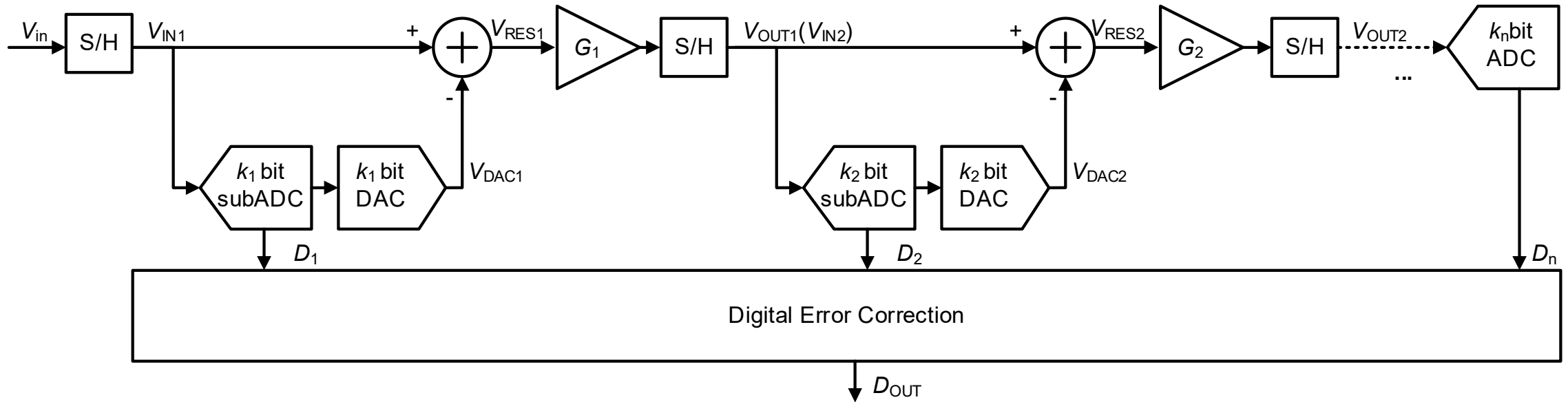

Basic Pipelined ADC

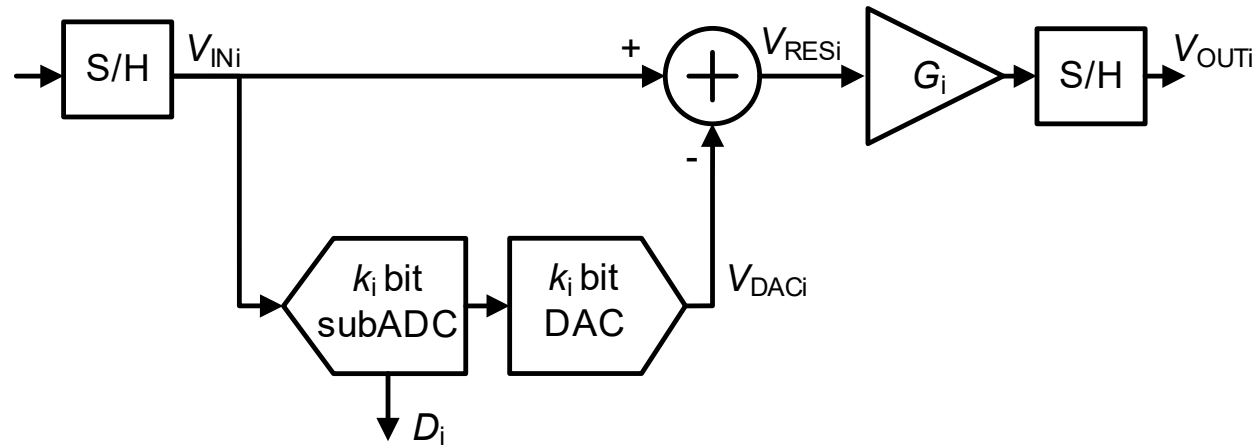- Differences between the Physical Model and the Actual Circuits



$$V_{OUTi} = G_i(V_{RESi}) = G_i(V_{INi} - V_{DACi}) = G_i(V_{INi} - \boxed{D_i} LSB_i) = G_i(V_{INi} - D_i \frac{V_{REF}}{2^{k_i-1}})$$


- In the circuits, the D_i in the formula is not equal to the digital output of the stage

Basic Pipelined ADC

- Differences between the Physical Model and the Actual Circuits


Physical Model:

- Magnitude from the **lower border**

 

Actual Circuits:

 
- Vector starting from the origin(**zero**)



- The key point is to build a **bijection** function between the input and output signal

Basic Pipelined ADC

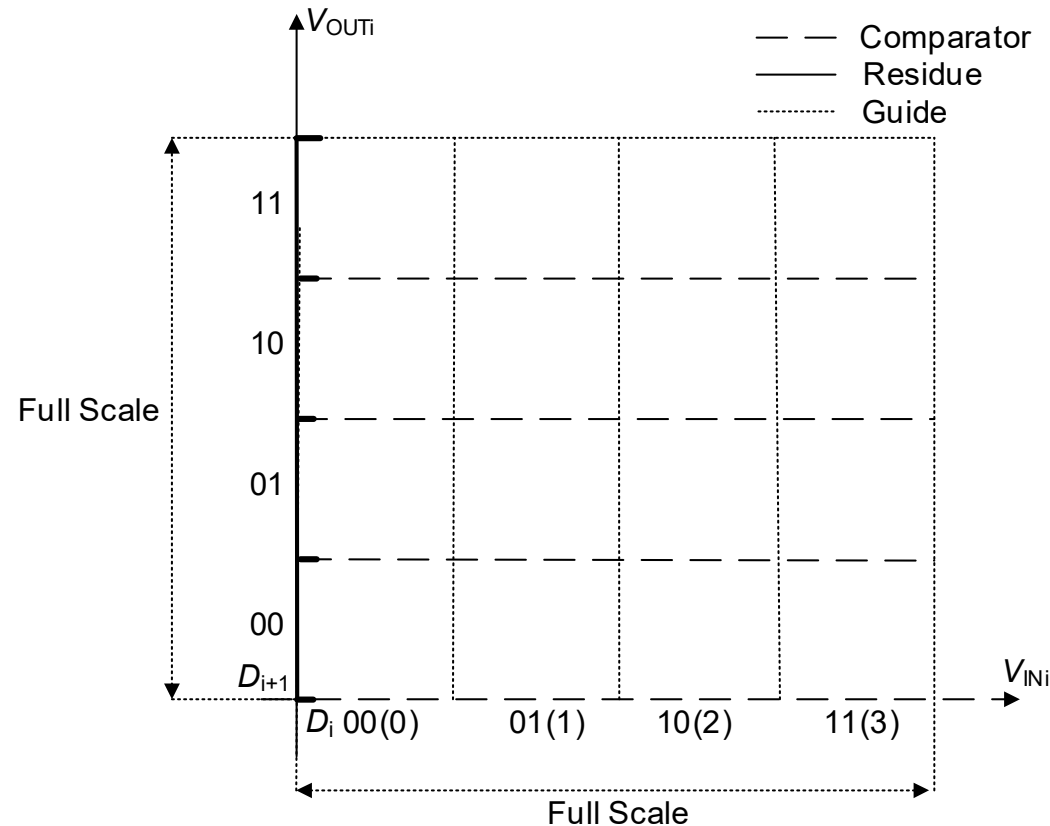
- The Requirements of the Transfer Waveform



- Sectional linear bijection function
- Output range is equal to input range

Basic Pipelined ADC


- Example 1

 

- The decoding is complex
- Voltage level changes more frequently

Basic Pipelined ADC

- Example 2

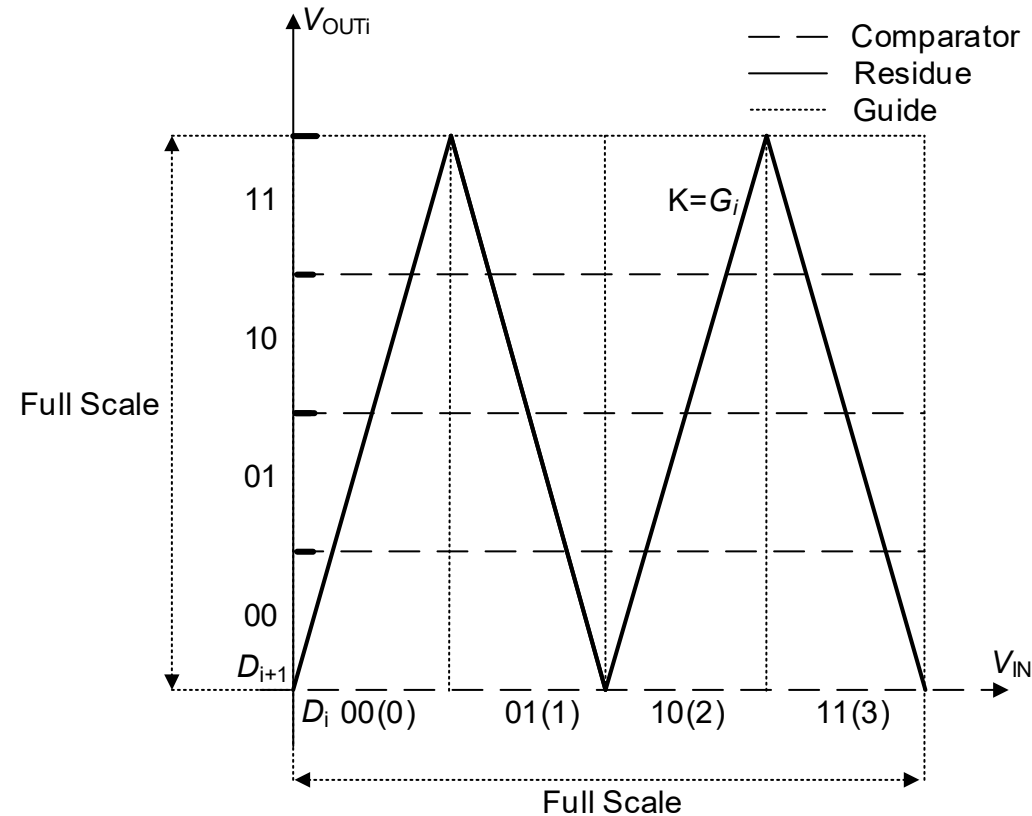

- Used in the folding ADC
- Unable to introduce the redundancy

- Example 3




Basic Pipelined ADC

- Differences between the Physical Model and the Actual Circuits


Physical Model:

- Magnitude from the **lower border**

 

Actual Circuits:

 
- Vector starting from the origin(**zero**)



- In the formula, the D_i should be written as D'_i
- D'_i is used to calculate the residue, D_i is the digital output of the stage
- D'_i may not be equal to D_i , but should be one-to-one corresponding to D_i

Basic Pipelined ADC

 - Math Expressions
- According to [two requirements](#) of transfer waveform, we can get the new curve:




- The formula:

$$V_{OUTi} = G_i(V_{INi} - V_{DACi}) = G_i(V_{INi} - D'_i \frac{V_{REF}}{2^{k_i-1}}) = G_i(V_{INi} - D'_i LSB_i)$$

Redundancy and Digital Error Correction

- Mismatch of Comparators

 


$$V_{OUT1} = 4(V_{IN1} - D'_1 LSB_1)$$

$$V_{OUT2} = 4(V_{OUT1} - D'_2 LSB_2)$$

Redundancy and Digital Error Correction

- Mismatch of Comparators

 

●: $V_{OUT2} = 16V_{IN1} - 16D'_1LSB_1 - 4D'_2LSB_2$

●: $V_{OUT2}^* = 16V_{IN1} - 16(D'_1+1)LSB_1 - 4(D'_2-3)LSB_2 = V_{OUT2} - 4LSB_2$

●: $D_{OUT} = 4D_1 + D_2$

●: $D_{OUT}^* = 4(D_1 + 1) + (D_2 - 3) = D_{OUT} + 1$

Redundancy and Digital Error Correction

- Problems Caused by the Mismatch
 - Amplified residue is out of the input range
 - Mismatch causes the error in the digital output and the next stage input

Redundancy and Digital Error Correction

- Solutions
 - Reduce the inter-stage gain and bring the redundancy
 - Correct the error in **the digital output** so the present output is right
 - Correct **the next stage input** so the later output is right

Redundancy and Digital Error Correction

- Solutions
 - Reduce the inter-stage gain and bring the redundancy
 - Correct the error in **the digital output** so the present output is right
 - Correct **the next stage input** so the later output is right
 - It can be proved that the next stage input is right when the digital output is right


$$\begin{aligned}V_{\text{OUT}2} &= G_2(V_{\text{IN}2} - D'_2 \text{LSB}_2) \\&= G_2(G_1 V_{\text{IN}1} - G_1 D'_1 \text{LSB}_1 - D'_2 \text{LSB}_2) \\&= G_2 \left[G_1 V_{\text{IN}1} - (G_1 2^{k_2 - k_1} D'_1 - D'_2) \text{LSB}_2 \right] \\&= G_2(G_1 V_{\text{IN}1} - \textcolor{red}{D'}_{\text{OUT}} \text{LSB}_2)\end{aligned}$$

Redundancy and Digital Error Correction

- Solutions
 - Reduce the inter-stage gain and bring the redundancy into residue
 - Correct the error in **the digital output** so the present output is right
 - Correct **the next stage input** so the later output is right
 - It can be proved that the next stage input is right when the digital output is right
 - In the following chapter, the analysis will only discuss about the digital error correction algorithm's effect on the digital output


Redundancy and Digital Error Correction

- Reduce the Inter-stage Gain

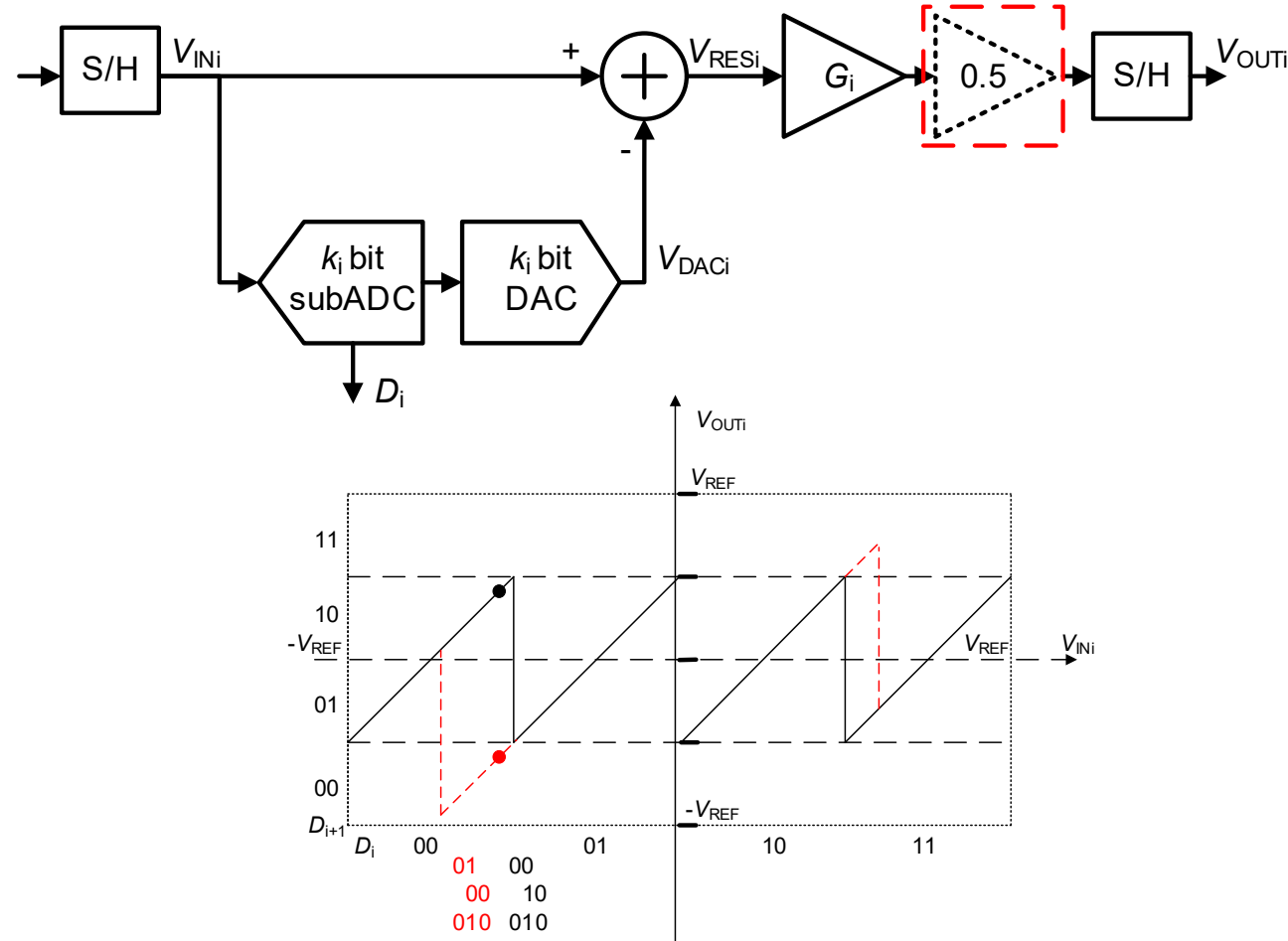

Redundancy and Digital Error Correction

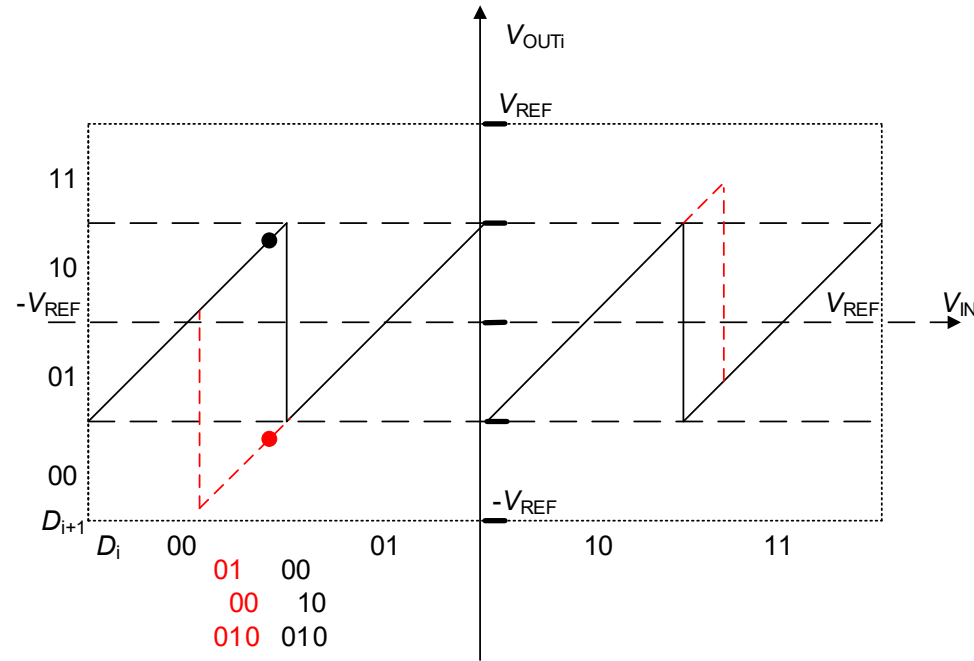- Digital Output of the Pipelined ADC with Redundancy




$$V_{OUTi} = G_i(V_{INi} - V_{DACi}) \quad G_1 = 2^{k_1-1}$$

$$D_{OUT} = G_1 2^{k_2-k_1} D_1 + D_2 = 2^{k_2-1} D_1 + D_2 = D_1 \ll \boxed{(k_2-1)} + D_2$$

1 bit overlap

Redundancy and Digital Error Correction

- Error Correction

 


$$V_{IN2} = V_{OUT1} = 4(V_{IN1} - D'_1 LSB_1)$$

$$D_1^* = D_1 + 1 \rightarrow V_{IN2}^* = V_{IN2} - 4LSB_1 \rightarrow D_2^* = D_2 - 3$$

$$D_{OUT} = 4D_1 + D_2$$
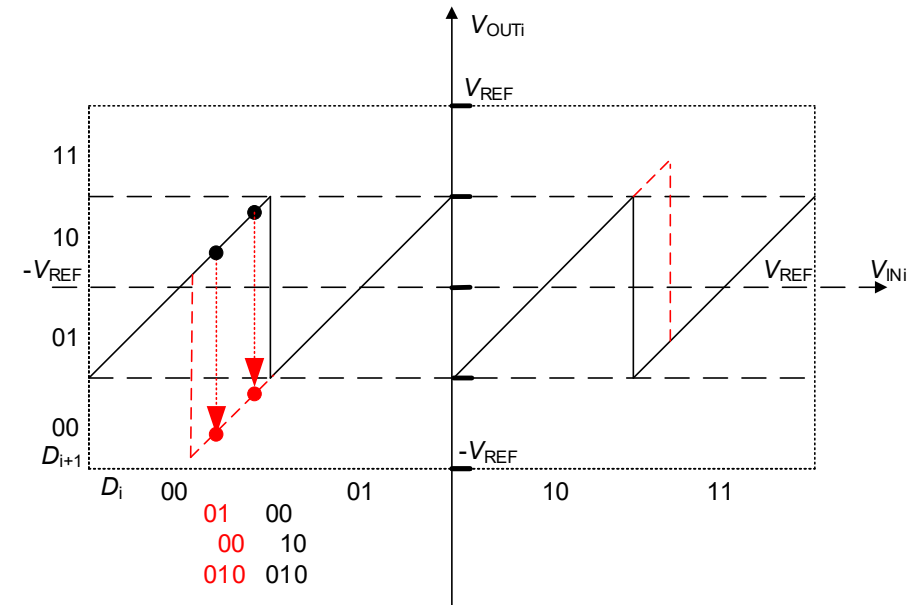
$$D_{OUT}^* = 4(D_1 + 1) + (D_2 - 3) = D_{OUT} + 1$$



$$V_{IN2} = V_{OUT1} = 2(V_{IN1} - D'_1 LSB_1)$$

$$D_1^* = D_1 + 1 \rightarrow V_{IN2}^* = V_{IN2} - 2LSB_1 \rightarrow D_2^* = D_2 - 2$$

$$D_{OUT} = 2D_1 + D_2$$

$$D_{OUT}^* = 2(D_1 + 1) + (D_2 - 2) = D_{OUT}$$

Redundancy and Digital Error Correction

- Key Points in the Correction
 - Digital output change can be fully detected
 - The weights ratio of digital output and its variation are intrinsically opposite

Redundancy and Digital Error Correction

- Key Points in the Correction
 - Digital output change can be **fully detected**
 - The weights ratio of digital output and its variation are **intrinsically opposite**

$$\begin{aligned} V_{\text{IN}i+1} &= V_{\text{OUT}i} = G_i(V_{\text{IN}i} - D'_i \text{LSB}_i) \\ \Delta D_1 \rightarrow \Delta V_{\text{IN}2} &= -G_1 \text{LSB}_1 \Delta D_1 \rightarrow \Delta D_2 = \frac{\Delta V_{\text{IN}2}}{\text{LSB}_2} \\ \Delta D_2 &= \frac{\Delta V_{\text{IN}2}}{\text{LSB}_2} = -\frac{G_1 \text{LSB}_1}{\text{LSB}_2} \Delta D_1 = -G_1 2^{k_2-k_1} \Delta D_1 = -\mathbf{W_{12}} \Delta D_1 \end{aligned}$$


Redundancy and Digital Error Correction

- Key Points in the Correction
 - Digital output change can be **fully detected**
 - The weights ratio of digital output and its variation are **intrinsically opposite**

$$\begin{aligned}\Delta D_2 &= -W_{12} \Delta D_1 \\ D_{\text{OUT}} &= G_1 2^{k_2-k_1} D_1 + D_2 = W_{12} D_1 + D_2 \\ D_{\text{OUT}}^* &= W_{12} (D_1 + \Delta D_1) + (D_2 + \Delta D_2) \\ &= W_{12} D_1 + D_2 + (W_{12} \Delta D_1 + \Delta D_2) \\ &= W_{12} D_1 + D_2 + (W_{12} \Delta D_1 - W_{12} \Delta D_1) \\ &= D_{\text{OUT}}\end{aligned}$$

Redundancy and Digital Error Correction

- Key Points: Recursive Thought

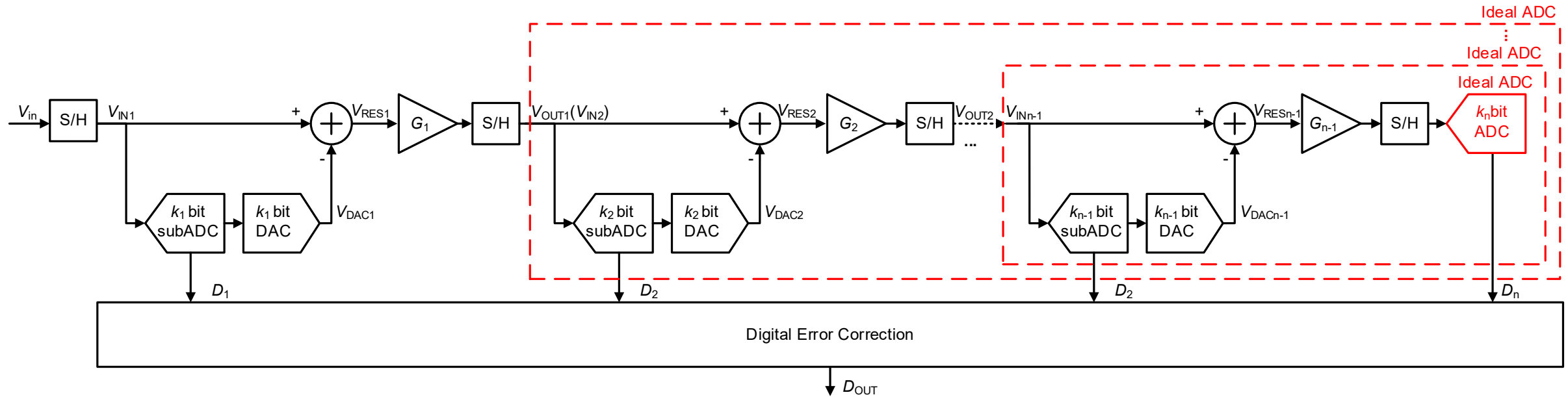


- Though the algorithm is discussed under the circumstance that there is no offset in the next stage's comparators, the algorithm remains feasible when the final stage is without or with little mismatch.

Comparator Offset and Digital Output

- Problems
 - Zero-cross comparator are sensitive to the noise (chatter)
 - The digital output has offset



Comparator Offset and Digital Output

- Digital Output Offset

 



Comparator Offset and Digital Output

- Offset Introduced to All Comparators

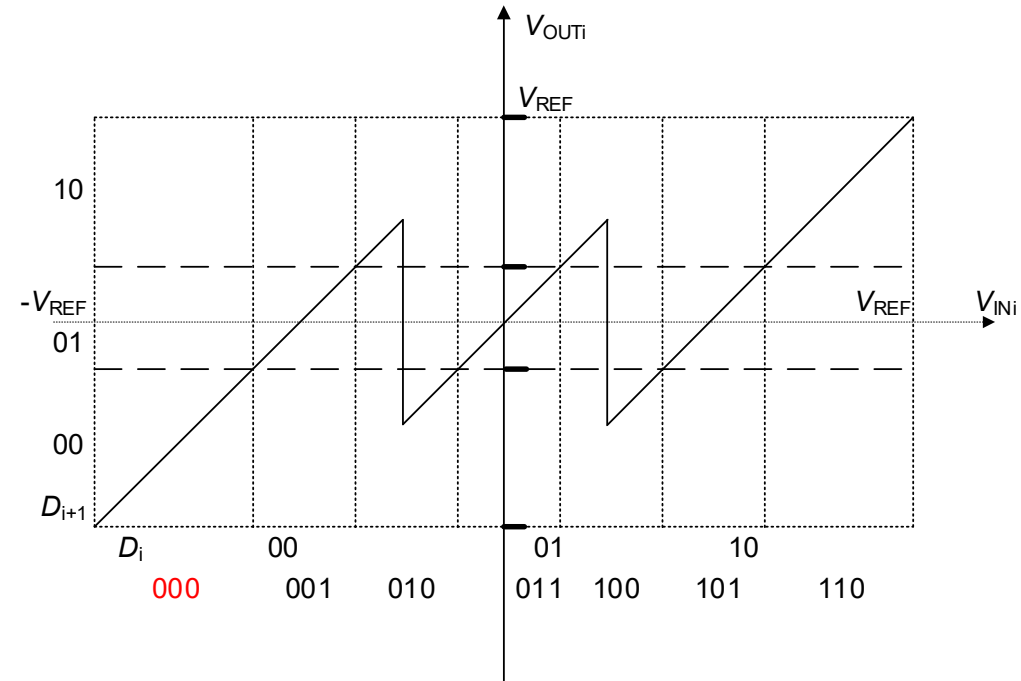 

Comparator Offset and Digital Output

- Error Correction

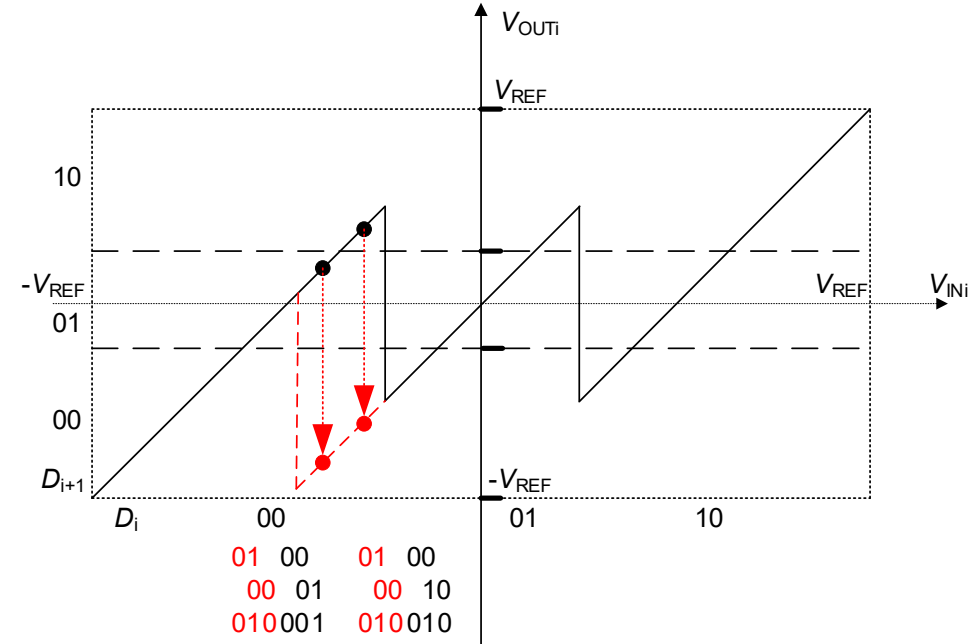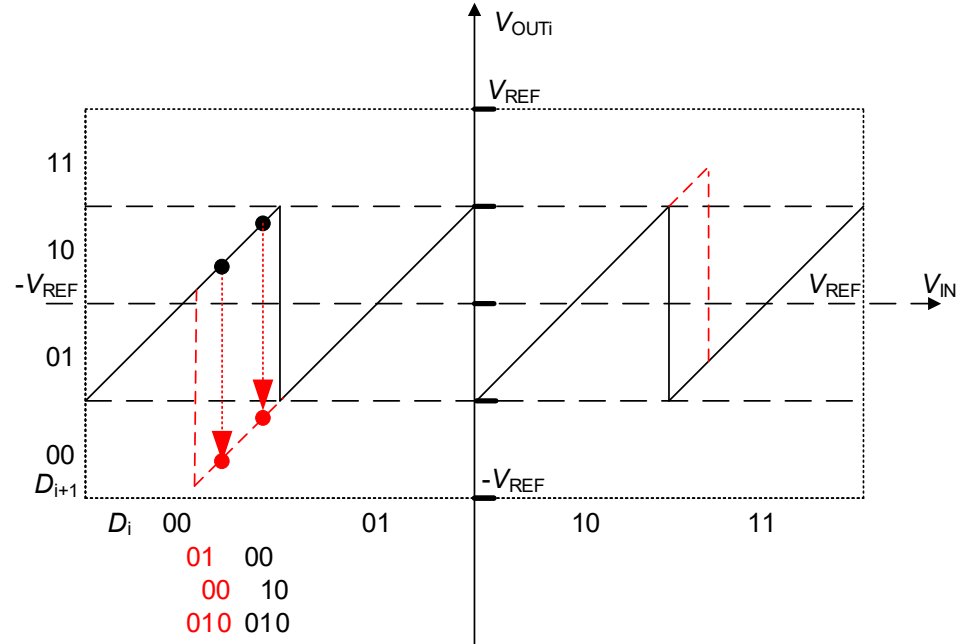


- The correction algorithm remains valid but some of the error are **not fully detected** (the arrow on the left only cross 1 comparators line instead of 2)

Comparator Offset and Digital Output

- Key Points in the Correction
 - Digital output change **can be fully detected**
 - The weights ratio of digital output and its variation are intrinsically opposite

Comparator Offset and Digital Output

- Error Correction

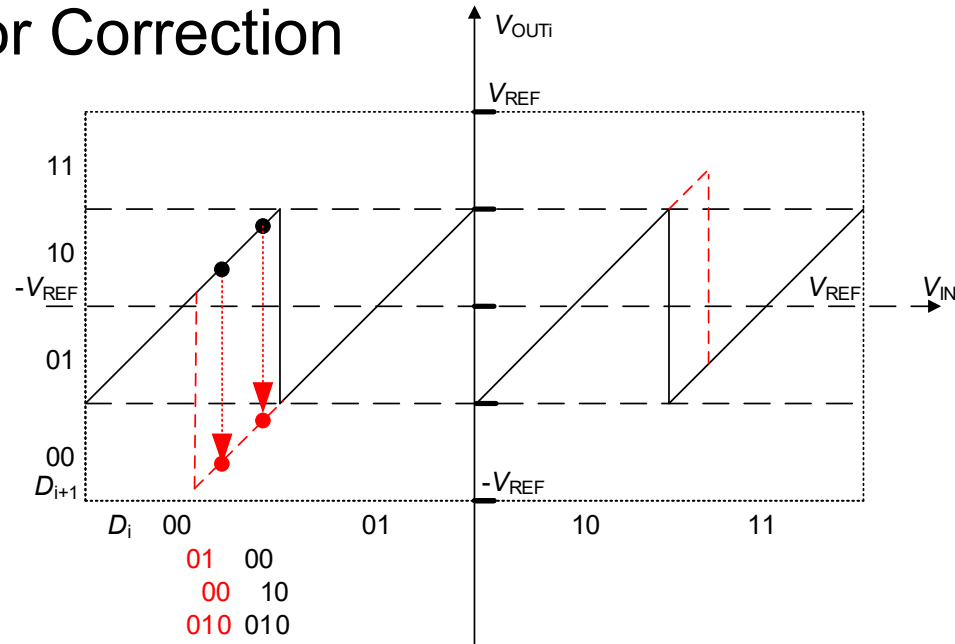


$$V_{IN2} = V_{OUT1} = 2(V_{IN1} - D'_1 LSB_1)$$

$$D_1^* = D_1 + 1 \rightarrow V_{IN2}^* = V_{IN2} - 2LSB_1 \rightarrow D_2^* = D_2 - 2$$

$$D_{OUT} = 2D_1 + D_2$$
 
$$D_{OUT}^* = 2(D_1 + 1) + (D_2 - 2) = D_{OUT}$$



$$V_{IN2} = V_{OUT1} = 2(V_{IN1} - D'_1 LSB_1)$$

$$D_1^* = D_1 + 1 \rightarrow V_{IN2}^* = V_{IN2} - 2LSB_1 \rightarrow D_2^* = D_2 - 1$$



$$D_{OUT} = 2D_1 + D_2$$

$$D_{OUT}^* = 2(D_1 + 1) + (D_2 - 1) = D_{OUT} - 1$$

- Error can't be corrected immediately

Comparator Offset and Digital Output



- Error Correction

  

- Generally, the final stage(stage n) is a zero-cross flash comparator and the error of the previous stage (stage $n-1$) **can be fully corrected**. The stage $n-1$ and stage n can be regarded as an ideal zero-cross flash together so all the previous error can be corrected (**recursive thought**) .

Comparator Offset and Digital Output

- Add a Comparator

 
 


- Error can't be corrected immediately

- Should be 1111(-1) instead of 0111(7)
- Error can be corrected immediately


Comparator Offset and Digital Output

- No Digital Output Offset

  


Redundancy and Digital Error Correction

 - The Correction Range (Tolerable Mismatch)
 - Example of a 3 bit stage with 2 bit overlap $k_i = 3$ $G_i = 2^{k_i-2}$




$$V_{Correcti} = V_{Redundancyi} / G_i$$

- 1.5 bit ?

 

 [1] S. H. Lewis, H. S. Fetterman, G. F. Gross, R. Ramachandran and T. R. Viswanathan, "A 10-b 20-Msample/s analog-to-digital converter," in IEEE Journal of Solid-State Circuits, vol. 27, no. 3, pp. 351-358, March 1992.



[2] S. Shin et al., "A 12 bit 200 MS/s Zero-Crossing-Based Pipelined ADC With Early Sub-ADC Decision and Output Residue Background Calibration," in *IEEE Journal of Solid-State Circuits*, vol. 49, no. 6, pp. 1366-1382, June 2014.

**Thanks for
Your Attention**